 


Jakub Bilski 155865

Podstawy Techniki Cyfrowej – lab nr 6



```
-- fourbit_counter.vhd
```

```
-- This is a simple 4-bit (Ripple) binary counter made up
```

```
-- of four T flip-flops. It also includes a clock divider
```

```
-- to bring down the input CK signal from 100 MHz to about 1 Hz.
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fourbit_counter is
```

```
    Port ( CK : in  STD_LOGIC;
```

```
          Q : out  STD_LOGIC_VECTOR (7 downto 0));
```

```
end fourbit_counter;
```

```
architecture Structural of fourbit_counter is
```

```
    component tff
```

```
        Port ( T    : in  STD_LOGIC;
```

```
              CK    : in  STD_LOGIC;
```

```
              Q, QN : out STD_LOGIC);
```

```
    end component;
```

```
    component ck_divider
```

```
        Port ( CK_IN : in  STD_LOGIC;
```

```

        CK_OUT : out STD_LOGIC);
end component;

signal all_T, S0, S1, s2, s3, s4, s5, s6, s7, internal_ck : STD_LOGIC;

begin

-- We use signal all_T set to logic '1' to drive
-- input T of all T flip-flops to logic '1'.
all_T <= '1';

CLOCK: ck_divider port map (CK, internal_ck);
TFF0: tff port map (all_T, internal_ck, Q(0), S0);
TFF1: tff port map (all_T, S0, Q(1), S1);
TFF2: tff port map (all_T, S1, Q(2), S2);
TFF3: tff port map (all_T, S2, Q(3), S3);
TFF4: tff port map (all_T, S3, Q(4), S4);
TFF5: tff port map (all_T, S4, Q(5), S5);
TFF6: tff port map (all_T, S5, Q(6), S6);
TFF7: tff port map (all_T, S6, Q(7), S

end Structural;

```